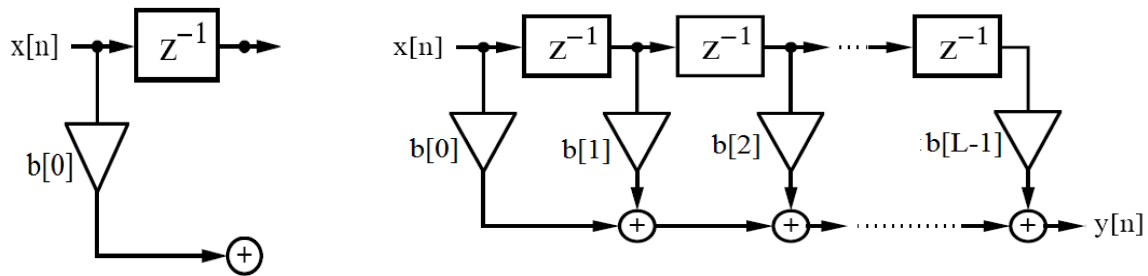


The finite impulse response (FIR) filter is a common component in many digital signal processing (DSP) systems. This implementation shows the basic FIR filter diagram with  $L$  length. The result of delays operates on input samples.

### Block Diagram:

For each integer  $n$ , the output is the values in the delay line scaled by  $b[0]$ ,  $b[1]$ , ...,  $b(L-1)$ .



### Process Map:

The FIR Filter implemented using three digital hardware elements including a Latch, a Multiplier and an Adder. The latch updates (Y) output using the value of the input (X).

